

# Hardware Connection Documentation

## Overview

This document details the connections between the ESP32-CAM and Arduino UNO for the smart recycling system. The system uses serial communication between the devices and controls various components including a servo motor, relay, TFT display, and a button.

## ESP32-CAM Connections

### Power

- VCC → 5V
- GND → GND

### Communication with Arduino UNO

- GPIO 12 (RX) → Arduino Pin 9 (TX)
- GPIO 13 (TX) → Arduino Pin 8 (RX)

### Button

- GPIO 4 → Button Pin
- Button GND → GND

### Relay Control for Arduino Power

- GPIO 14 → Relay Control Signal
- Base of PN2222A Transistor → GPIO 14 via 1kΩ Resistor
- Base of PN2222A Transistor → GND via 20kΩ Resistor
- Emitter of PN2222A → GND
- Collector of PN2222A → Relay Module IN Pin

### Camera Module

The camera module is directly integrated into the ESP32-CAM board.

## Arduino UNO Connections

### Power

- Vin → ESP32 Relay NC 1
- GND → ESP32 Relay NC 2

### TFT Display

- CS → A5
- CD → A3
- RST → A4
- LED → A0
- VCC → 5V
- GND → GND

### Servo Motor

- Signal → Pin 7
- VCC → 5V
- GND → GND

### Relay

- Control → Pin 6
- VCC → 5V
- GND → GND

## Charger

- 5v positive → Relay NC
- GND → GND

## Communication with ESP32-CAM

- Pin 8 (RX) → ESP32-CAM GPIO 13 (TX)
- Pin 9 (TX) → ESP32-CAM GPIO 12 (RX)

## Communication Protocol

- Baud Rate: 9600
- Data Format: 8N1 (8 data bits, no parity, 1 stop bit)

## System Operation Flow

### 1. Initial State

- ESP32-CAM waits for button press
- Arduino displays welcome message on TFT

### 2. When Button Pressed

- ESP32-CAM captures image
- Processes image through Edge Impulse model
- Sends classification result to Arduino

### 3. Arduino Response

- If plastic bottle detected:
  - Servo moves to accept position
  - Activates charging relay
  - Displays charging status
- If non-plastic item detected:
  - Servo moves to reject position
  - Displays rejection message

### 4. Charging Cycle

- 15-minute timer starts
- TFT displays countdown
- System returns to initial state after completion

## Important Notes

### 1. Power Supply

- Both devices need stable 5V power supply
- Consider separate power supply for servo if using larger model

### 2. Ground Connection

- All grounds (GND) should be connected together
- This ensures proper communication and operation

### 3. Serial Communication

- Communication is bidirectional
- ESP32-CAM sends classification results
- Arduino sends charging status updates

### 4. Safety Considerations

- Double-check all connections before powering on
- Ensure proper insulation of all connections
- Monitor system temperature during operation

### 5. Serial Communication Conflict

- The ESP32-Cam must boot first before the Arduino to avoid conflict in Serial Communication
- Relay is added to power the Arduino so that it won't boot while ESP32-Cam is booting or else it cause error to the ESP32-Cam

# Troubleshooting Tips

## 1. If Communication Fails

- Verify TX/RX connections are correct
- Confirm baud rate settings match (9600)
- Check ground connections

## 2. If Servo Doesn't Respond

- Verify 5V power is sufficient
- Check signal wire connection
- Confirm servo library is properly initialized

## 3. If TFT Display Issues

- Verify SPI connections
- Check power supply voltage
- Confirm library configuration matches connections

## 4. If Camera Doesn't Work

- Check camera module connection
- Verify ESP32-CAM initialization
- Confirm proper power supply